Advanced Computer Architecture

Lecture No. 35

Reading Material

Vincent P. Heuring & Harry F. Jordan Computer Systems Design and Architecture Chapter 6 6.3, 6.4

Summary

- Overflow
- Different Implementations of the adder
- Unsigned and Signed Multiplication
- Integer and Fraction Division
- Branch Architecture

Overflow

When two m-bit numbers are added and the result exceeds the capacity of an m-bit destination, this situation is called an overflow. The following example describes this condition:

Example 1

Overflow in fixed point addition:

Base 2	Base 8	Base 16	
1011.1	7.25	C36.A	
+1110.0	+6.76	+72B.3	
c 1100 s 11001.1	c <u>11 .1</u> s <u>16.23</u>	c <u>1010</u> s 1361.D	

In these three cases, the fifth position is not allowed so this results in an overflow.

Different Implementations of the Adder

For a binary adder, the sum bit is obtained by following equation:

 $s_{j} = x_{j}y_{j}c_{j} + x_{j}y_{j}c_{j} + x_{j}y_{j}c_{j} + x_{j}y_{j}c_{j}$ and the equation for carry bit is $c_{j+1} = x_{j}y_{j} + x_{j}c_{j} + y_{j}c_{j}$ where x and y are the input bits. The sum can be computed by the two methods:

- Ripple Carry Adder
- Carry Look ahead Adder

Ripple Carry Adder

In this adder circuit, we feed carry out from the previous stage to the next stage and so on. For 64 bit addition, 126 logic levels are required between the input and output bits. The logic levels can be reduced by using a higher base (Base 16). This is a relatively slow process.

Complement Adder/Subtractor

We can perform subtraction using an unsigned adder by

- Complement the second input
- Supply overflow detection hardware

2's Complement Adder/Subtractor

A combined adder/subtractor can be built using a mux to select the second adder input. In this case, the mux also determines the carry-in to the adder. The equation for mux output is :

$$q_j = y_j \overline{r} + \overline{y_j} r$$

Carry Look ahead Adder

The basic idea in carry look ahead is to speed up the ripple carry by determining whether the carry is generated at the j position after addition, regardless of the carry-in at that stage or the carry is propagated from input to output in the digit.

This results in faster addition and lesser propagation delay of the carry bits. It divides the carry into two logical variables G_j (generate) and P_j (propagate). These variables are defined as:

$$G_{j} = x_{j} y_{j}$$
$$P_{j} = x_{j} + y_{j}$$

Hence the carry out will be

$$c_{j+1} = G_j + P_j c_j$$

Here the G and P each require one gate, and the sum bit needs two more gates in the full adder. This results in a less complexity i.e. log(m) which is much less as compare to ripple carry adder where complexity is m (m is the number of bits of a digit to be added). Ripple carry and look ahead schemes are can be mixed by producing a carry-out at the left end of each look ahead module and using ripple carry to connect modules at any level of the look ahead tree.

Unsigned Multiplication

The general schema for unsigned multiplication in base b is shown in Figure 6.5 of the text book.

Parallel Array Multiplier

Figure 6.6 of the text book shows the structure of a fully parallel array multiplier for base b integers. All signal lines carry base b digits and each computational block consists of a full adder with an AND gate to form the product x_iy_j . In case of binary, m² full adders are required and the signals will have to pass through almost 4m gates.

Series parallel Multiplier

A combination of parallel and sequential hardware is used to build a multiplier. This results in a good speed of operation and also saves the hardware.

Signed Multiplication

The sign of a product is easily computed from the sign of the multiplier and the multiplicand. The product will be positive if both have same sign and negative if both have different sign. Also, when two unsigned digits having m and n bits respectively are multiplied, this results in a (m+n) –bit product, and (m+n+1)-bit product in case of sign digits. There are three methods for the multiplication of sign digits:

- 1. 2's complement multiplier
- 2. Booth recoding
- 3. Bit-Pair recoding

2's complement Multiplication

If numbers are represented in 2's complement form then the following three modifications are required:

- 1. Provision for sign extension
- 2. Overflow prevention
- 3. Subtraction as well as addition of the partial product

Booth Recoding

The Booth Algorithm makes multiplication simple to implement at hardware level and speed up the procedure. This procedure is as follows:

- 1. Start with LSB and for each 0 of the original number, place a 0 in the recorded number until a 1 in indicated.
- 2. Place a 1 for 1in the recorded table and skip any succeeding 1's until a 0 is encountered.
- 3. Place a 0 with 1 and repeat the procedure.

Example 2

Recode the integer 485 according to Booth procedure.

Solution

Original number: 00111100101=256+128+64+32+4+1=485 Recoded Number:

01000101111=+512-32+8-4+2-1=485

Bit-Pair Recoding

Booth recoding may increase the number of additions due to the number of isolated 1s. To avoid this, bit-pair recoding is used. In bit-pair recoding, bits are encoded in pairs so there are only n/2 additions instead of n.

Division

There are two types of division:

- Integer division
- Fraction division

Integer division

The following steps are used for integer division:

- 1. Clear upper half of dividend register and put dividend in lower half. Initialize quotient counter bit to 0
- 2. Shift dividend register left 1 bit
- 3. If difference is +ve, put it into upper half of dividend and shift 1 into quotient. If ve, shift 0 into quotient
- 4. If quotient bits<m, goto step 2
- 5. m-bit quotient is in quotient register and m-bit remainder is in upper half of dividend register

Example 3

Divide 4710 by 510.

Solution

```
D=000000 101111, d=000101
D 000001 011110
d 000101
Diff(-) q 0
D 000010 111100
```

Advanced Computer Architecture-CS501

d	000101		
Diff(-)		q	00
D	000101 111000		
d	000101		
Diff(+)		q	001
D	000001 110000		
d	000101		
Diff(-)		q	0010
D	000011 100000		
d	000101		
Diff(-)		q	00100
D	000111 000000		
d	000101		
Diff(+)	000010	q	001001

Hence remainder = $(000010)_2 = 2_{10}$ Quotient = $(001001)_2 = 9_{10}$

Fraction Division

The following steps are used for fractional division:

- 1. Clear lower half of dividend register and put dividend in upper half. Initialize quotient counter bit to 0
- 2. If difference is +ve, report overflow
- 3. Shift dividend register left 1 bit
- 4. If difference is +ve, put it into upper half of dividend and shift 1 into quotient. If negative, shift 0 into quotient
- 5. If quotient bits<m, go to step 3
- 6. m-bit quotient has decimal at the left end and remainder is in upper half of dividend register

Branch Architecture

The next important function perform by the ALU is branch. Branch architecture of a machine is based on

- 1. condition codes
- 2. conditional branches

Condition Codes

Condition Codes are computed by the ALU and stored in processor status register. The 'comparison' and 'branching' are treated as two separate operations. This approach is not used in the SRC. Table 6.6 of the text book shows the condition codes after subtraction, for signed and unsigned x and y. Also see the SRC Approach from text book.

Usually implementation with flags is easier however it requires status registers. In case of branch instructions, decision is based on the branch itself.

Note: For more information on this topic, please see chapter 6 of the text book.